

## ANNA UNIVERSITY QUESTIONS

### COMBINATIONAL LOGIC

#### PART-A

1. What are half and full adders? (April 2003)
2. State the condition for  $B = I_2$  in the Boolean expression  

$$B = I_0 \bar{S}_0 \bar{S}_1 + I_1 \bar{S}_0 S_1 + I_2 S_0 \bar{S}_1 + I_3 S_0 S_1$$
(April 2003)  
 What is the combinational logic circuit realised by the above boolean expression.
3. State the condition to check the equality of two n-bit binary numbers A and B. (April 2003)
4. Distinguish between combinational and sequential logic circuits. (April 2003, April 2004)
5. Using a single 7485 IC, draw the logic diagram of a 4 bit comparator. (April 2003)
6. Write down the truth table of a full adder. (April 2004)
7. Write down the truth table of a full subtractor. (Nov. 2004)
8. Describe the truth table of a half subtractor and write the Boolean expression corresponding to the difference and the borrow. (April 2005)
9. What is a combinational circuit? Give an example. (April 2005)
10. Draw the circuit of a half-adder. (Dec. 2005)
11. Write the truth table for a half-subtractor. (Dec. 2005)
12. Draw the flow diagram of gray to binary conversion. (Dec. 2005)
13. Draw a combinational logic circuit which can compare whether two bit binary numbers are same or not. (Dec. 2005)
14. Draw a parity checker circuit for 3 bit binary word  $x_1 x_2 x_3$ . (May 2006)
15. Represent a half adder in block diagram form and also its logic implementation. (May 2006)
16. Construct a 4-bit binary to gray code converter circuit and discuss its operation. (May 2006)
17. Mention any two uses of HDL. (May 2006)
18. What is logic synthesis? (Dec. 2006)
19. List the important features of HDL. (Dec. 2006)
20. Design a half adder. (May 2007)
21. What is a full adder? (May 2007)
22. What are the modeling techniques available to build HDL module? (May 2007)
23. Draw the circuit diagram for 3 bit parity generator. (Dec. 2007)
24. Define combinational circuit. (May 2009)

25. What is the need for code conversion? Give two commonly used codes. (May 2009)

**PART-B**


1. Design a parity generator to generate an odd parity bit for a 4-bit word. Use EX-OR and EX-NOR gates. (8) (April 2003)
2. Design a combinational circuit that compares two 4-bit numbers A and B to check if they are equal or not. (8) (April 2003)
3. (i) Design a full adder and a full subtractor. (14)  
(ii) Draw the block diagram of a 2's complement adder/subtractor. (2) (April 2003)
4. Using a single 7483, draw the logic diagram of a 4 bit adder/subtractor.
5. Draw the Logic diagram of a 4 bit parallel adder/subtractor using full adders and explain. (8) (Nov. 2003)
6. Draw a full adder circuit using only NOR gates. (8) (Nov. 2003)
7. Design and explain the following circuits: (i) Full adder, (ii) Comparator. (16) (Nov. 2003)
8. (i) Explain how a full adder can be built using two half adders and an OR gate. (6)  
(ii) Design a half adder using atmost three NOR gates. (10) (April 2004)
9. Design a look ahead carry generator. (16) (April 2004)
10. Design a circuit that converts 8421 BCD Code to excess 3 code. (16) (April 2004)
11. Implement the logic function  $Y(A, B, C) = \sum m(1, 2, 7)$  using 74151A and 74153. (8) (Nov. 04)
12. Design a Binary to Gray Converter. (16) (Nov. 2004)
13. Design a BCD to Gray Code Converter. Use don't cares. (16) (Nov. 2004)
14. Explain carry look ahead adder circuit. (16) (Nov. 2004)
15. Explain with truth table and gate level circuit diagram for a full adder. (12) (April 2005)
16. Design a combinational circuit which accepts 3 bit binary number and converts its equivalent excess 3 code. (10) (April 2005)
17. Design and explain the working of Gray to BCD converter. (16) (April 2005)
18. Design a BCD adder to add two BCD digits. (16) (Dec. 2005)
19. (i) Design a 4-bit binary to BCD code converter. (10) (Dec. 2005)  
(ii) Design a 4-bit binary to gray code converter. (6) (Dec. 2005)
20. Design and implement a binary to gray code converter. (16) (Dec. 2005)
21. Design a combinational circuit whose input is 4 bit binary number and whose output is 2's complement of input number. (4) (Dec. 2005)
22. Design a combinational logic circuit that will generate the square of all the combinations of a 3 bit binary number. (8) (Dec. 2005)
23. Design and explain: (i) 4 bit magnitude comparator. (16) (May 2006)

- 
24. Design a BCD to 7 segment code converter. (16) (May 2006)
25. (i) Design a binary multiplexer, using half adders and/or full adders, to multiply two 2-bit numbers. (8)
- (ii) Design a combinational logic circuit to compare two 2-bit binary numbers A and B and to generate the outputs  $A < B$ ,  $A = B$  and  $A > B$ . Is there a way to derive the third output from the first two outputs? (8) (May 2006)
26. Design a 4 bit magnitude comparator to compare two 4 bit numbers. (16) (Dec. 2006)
27. Construct a combinational circuit to convert given binary coded decimal number into an Excess-3 code. For example when the input to the gate is 0110 then the circuit should generate output as 1001. (16) (Dec. 2006)
28. Design a 4 bit comparator using logic gates. (16) (May 2007)
29. Design a 4 bit adder/subtractor using logic gates and explain its operation. (16) (May 2007)
30. Draw the block diagram of a BCD adder and explain its operation. (10) (May 2007)
31. (i) Design a combinational circuit to convert BCD to gray code. (12) (May 2007)
- (ii) Design a 4 bit subtractor. (4) (May 2007)
32. (i) Design a combinational circuit to convert Excess-3 code to BCD code. (10) (May 2007)
- (ii) Design a 2 bit x 2 bit multiplier. (6) (May 2007)
33. (i) Design a combinational circuit to convert gray code to BCD. (12) (Dec. 2007)
- (ii) Design a Full adder circuit with a Decoder. (4) (Dec. 2007)
34. Design a 4 bit magnitude comparator to compare two 4 bit numbers. (Dec. 2007)
35. (i) Design a combinational circuit with three inputs and one output. The output is 1 when the binary value of the inputs is less than three. The output is 0 otherwise. (6) (Dec. 2008)
- (ii) Design a code converter that converts a decimal digit from 8, -4, -2, -1 code to BCD. (10) (Dec. 2008)
36. (i) Design a 4 bit combinational circuit incrementer – A circuit that adds one to a 4-bit binary number? Use half-adders for this problem. (8) (Dec. 2008)
- (ii) Design a combinational circuit that generates the 9's complement of a BCD digit. (8) (Dec. 2008)
37. Design a BCD to 7 segment decoder. (16) (May 2009)
38. With a suitable block diagram explain the operation of BCD adder. (16) (May 2009)

## COMBINATIONAL LOGIC

### PART-A

 1. Distinguish between a decoder and a multiplexer. (Nov 2003, April 2004)
2. Draw a 1 to 2 demultiplexer circuit. (Nov 2003)
3. Draw a 1 to 2 multiplexer circuit. (Nov 2003)
4. What is a demux? (April 2004)
5. What is a decoder and obtain the relation between the number of inputs 'n' and outputs 'm' of a decoder? (April 2005)
6. Implement the logic function  $f = AB + A'B$  using a suitable multiplexer. (Dec 2005)
7. How can a decoder be converted into a demultiplexer? (Dec 2005)
8. Distinguish between decoder and multiplexer. (Dec 2005)
9. Implement the logic function  $f = \sum m(0,2,3,6)$  using a decoder. (May 2006)
10. How can a multiplexer used to convert 8-bit parallel data into serial form? (May 2006)
11. What are functions of encoders and decoders? (Dec. 2006)
12. What is a Multiplexer? (Dec. 2006)
13. Design a 2 input NAND gate using 2:1 multiplexer. (May 2007)
14. Implement the given function in 4:1 multiplexer  $f = \sum m(0,1,3,5, 6)$ . (May 2007)
15. What is a priority encoder? (May 2007)
16. Mention any two applications of multiplexers. (May 2007)
17. What is logic syntheses in HDL? (Dec. 2007)
18. Construct a 16x1 multiplexer with two 8x1 multiplexer and 2x1 multiplexer. (Dec. 2008)
19. Draw the logic diagram of 4 bit even parity checker. (Dec. 2008)
20. What is decoder? Draw the block diagram and truth table for 2 to 4 decoder. (May 2009)
21. Give some applications of multiplexer. (May 2009)
22. Compare the serial and parallel adder. (Dec 2010)
23. Define look ahead carry addition. (Dec 2010)
24. Define priority encoder (Dec 2010)
25. Write a dadflow description of a 2-to-1 line Mux uisng a condiitonal operator (Dec 2010)
24. Draw the schematic of half-adder logic. (May 2011)
25. Determine the size and number of multiplexers required to implement a full adder. (May 2011)
26. Write the HDL description of the following circuit. (May 2011)



27. With a block diagram show how a full adder can be designed using two half adders and one OR gate. (Dec 2011)
28. List the modelling techniques available in HDL. (Dec 2011)
29. Define decoder. Draw the block diagram and truth table for 2 to 4 decoder. (Dec 2011)
30. Define Tri-state gates. (May 2012)
31. Define Logic Synthesis and Simulation. (May 2012)
32. Write the stimulus for 2-to-1 line multiplexer. (May 2012)
33. Implement a Full adder with two half adders. (Dec 2012)
34. Implement a 4-bit even parity checker. (Dec 2012)
35. Construct a  $4 \times 16$  decoder using  $3 \times 8$  decoders. (Dec 2012)
36. Write down the truth table of a full subtractor. (May 2013)
37. What is meant by Test Bench? (May 2013)
38. Distinguish between a decoder and a demultiplexer. (May 2013)

**PART – B**

1. Implement the function  $F(X_1, X_2, X_3, X_4) = \sum (0, 1, 3, 4, 8, 9, 15)$  with an  $8 \times 1$  multiplexer where the following variables are connected in the specified order to selection lines  $S_2, S_1$  and  $S_0$  respectively (i)  $X_1, X_2, X_3$  (ii)  $X_2, X_3, X_4$  (8) (April 2003)
2. Design and explain the working of a 1 to 8 demultiplexer. (10) (April 2003)
3. Explain how you will build a 64 input MUX using nine 8 input MUXs. (8) (April 2003)
4. Implement the following Boolean function using an 8 to 1 multiplexer and 4 to 1 multiplexer.  $F(A, B, C) = \sum (0, 1, 5, 7)$ . (12) (Nov 2003)
5. Design and explain the working of a 4 to 1 multiplexer. (8) (Nov 2003)
6. Realize  $F(w, x, y, z) = \sum (1, 4, 6, 7, 8, 9, 10, 11, 15)$  using 4 to 1 MUX. (16) (April 2004)
7. (i) Implement a 3 to 8 line decoder. (8)


- (ii) Implement the logic function  $Y(A,B,C) = \sum m(1,2,7)$  using 74151A and 74153.  
(8) (Nov 2004)
8. Design a seven segment decoder circuit to display the numbers 0 to 3. (16) (Nov 2004)
9. Implement the switching function  $F = \sum (3, 6-8, 10, 13-15)$  using an 8 input multiplexer.  
(10) (Nov 2004)
10. Show that when two 2 input multiplexers drive another 2 input MUX, the result is a 4 input multiplexer.  
(6) (Nov 2004)
11. Show that when a 3 line to 8 line DEMUX drives eight 3 line to 8 line DEMUXs, the result is a 6 line to 64 line DEMUX.  
(6) (Nov 2004)
12. Implement the following function with a multiplexer,  $f(a,b,c,d) = \sum (0,1, 3,4,8,9,15)$ .  
(10) (April 2005)
13. Implement the following Boolean expression using an 4:1 MUX  $F = \sum (0,1, 2,4,6,9,12,14)$ .  
(8) (April 2005)
14. Design and explain the working of full adder and a decoder. (12) (April 2005)
15. What is the simplest logic circuit for a decoder that produces a 1 output when the BCD input is 0000 ?  
(8) (Dec 2005)
16. Implement the following function with a multiplexer,  $f(A,B,C,D) = \sum (0,1, 3,4,8,9,15)$ .  
(6) (Dec 2005)
17. Write the structural VHDL description for a 2 to 4 decoder and explain it in detail.  
(16) (Dec 2005)
18. Implement the following Boolean function using an 8:1 MUX  $f(a,b,c,d) = a'bd' + acd + b'cd + a'c'd$   
(8) (Dec 2005)
19. Design and explain the priority encoder. (8) (May 2006)
20. Describe the structural verilog description of 4 to 1 multiplexer. Also draw the internal diagram of the multiplexer.  
(16) (May 2006)
21. Construct a full adder circuit and write a HDL program module for the same.  
(16) (Dec. 2006)
22. (i) Implement the following with a multiplexer  
 $F(A,B,C) = \sum(1,2,4,5)$  (8) (Dec. 2006)
23. Implement the Boolean function using 8:1 multiplexer.  
 $F(A,B,C,D) = A'BD + ACD + B'CD + A'C'D$ . (8) (May 2007)

24. Construct a full adder circuit and write a HDL program module for the same.  
(16) (May 2007)
25. Implement the Boolean function using 8:1 multiplexer.  

$$F(A,B,C,D) = AB'D + A'C'D + B'CD' + AC'D.$$
(16) (Dec. 2007)
26. (i) A 8x1 multiplexer has inputs A,B and C connected to the selection inputs S2, S1 and S0 respectively. The data inputs 10 to 17 are as follows 11=12=17=0; 13=15=15=1; 10=14=D and 16=D'. Determine the Boolean function that the multiplexer implements.  
(10) (Dec. 2008)
- (ii) Write the HDL dataflow description of a quadrupul –2 to –1 line multiplexers with enable.  
(6) (Dec. 2008)
27. (i) using the conditional operator (?;), write a HDL, dataflow description of a 4-bit adder subtractor of unsigned numbers.  
(8) (Dec. 2008)
- (ii) Implement the Boolean function  $F = \Sigma(0,1,3,4,8,9,15)$  using a multiplexer.  
(8) (Dec. 2008)
28. Define decoder. Design a 3 to 8 decoder. With suitable block diagram explain how a 4 to 16 decoder can be formed by using the same.  
(16) (May 2009)
29. Relative a BCD to Excess-3 code conversion circuit starting from its truth table.  
(16) (Dec 2010)
30. Design a full adder and subtractor using NAND and NOR gates respectively.  
16 (Dec. 2010)
31. (i) Define multiplexer  
(ii) Implemment the following Boolean function using 8 : 1 MUX.  

$$F(A, B, C, D) = ABC + ACD + BCD + ACD$$
16 (Dec. 2010)
32. (i) Design a combinational circuit that comprises only of NOR gates for the following expression giving the input output relation.  
(10)
- (ii) Draw the schematic of a full adder circuit and give its truth table. (6) (May 2011)
33. (i) Design a BCD to Excess - 3 code converter using truth table and K-Map simplification  
(10) (May 2011)
- (ii) Draw the schematic of a magnitude comparator and give its truth table.  
(6) (May 2011)

 34. (i) Design a combinational logic using a suitable multiplexer to realize the following Boolean expression. (10)
- (ii) Compare and contrast between encoders and multiplexers. (6) (May 2011)
35. Consider the combinational circuit shown in figure.




- (i) Derive the Boolean expressions for  $T_1$  through  $T_4$ . Evaluate the outputs  $F_1$  and  $F_2$  as a function of the four inputs. (4)
- (ii) List the truth table with 16 binary combinations of the four input variables. Then list the binary values for  $T_1$  through  $T_4$  and outputs  $F_1$  and  $F_2$  in the table. (4)
- (iii) Plot the output Boolean function obtained in part (ii) on maps and show that simplified Boolean expressions are equivalent to the ones obtained in Part (i) (8) (Dec. 2011)
36. (i) With suitable block diagram explain Binary multiplier. (8)
- (ii) Write a detailed note on carry-propagation. (8) (Dec. 2011)
37. Construct a 5 to 32 line decoder with four 3 to 8 line decoders with enable and a 2 to 4 line decoder. Use block diagrams for components. (16) (Dec. 2011)
38. (i) Implement the following Boolean function with 16 x 1 multiplexer : (6)



$$F(A, B, C, D) = \sum(0, 1, 3, 4, 8, 9, 15)$$

Use block diagram representation.

 - (ii) Write HDL gate level description for 3 to 8 line decoder. (4) (Dec. 2011)
39. Design Half and Full Subtractor circuits. (16) (May 2012)
40. Design a circuit that converts 8421 BCD code to Excess-3 code. (16) (May 2012)
41. Implement a full adder with two  $4 \times 1$  multiplexers. (16) (May 2012)
42. i) Analyse the combinational circuit shown in figure, determine the truth table and the Boolean expressions governing the outputs of the circuit. (10)



- ii) Explain BCD adder with a neat block diagram. (6) (Dec 2012)
43. i) Design a BCD to excess-3 code converter using logic gates. (12)
- ii) Draw the diagram of a 4-bit adder subtractor using full adder. (4) (Dec 2012)
44. Implement  $F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$  using  $8 \times 1$  multiplexer. (8) (Dec 2012)
45. Design a 4-input priority encoder. (6) (Dec 2012)
46. Design a full adder using 2 half adders. (16) (May 2013)
47. Design a combinational circuit to convert binary to gray code. (16) (May 2013)
48. Implement the switching function  $F = \sum m(0, 1, 3, 4, 12, 14, 15)$  using an 8 input MUX. (16) (May 2013)